

# NCTU-EE IC LAB – Fall 2024

## Lab01 Exercise

### Design: Snack Shopping Calculator(SSC)

#### Data Preparation

1. Extract files from TA's directory:  
`% tar -xvf ~iclabTA01/Lab01.tar`

#### Design Description and Examples

One day, the professor asks you to buy some snacks for your lab. He/She gives you a credit card to let you buy the snacks. Also, the professor gives you a list of several choices of snacks, each with a different price and amount needed. However, you're not sure if this credit card is valid or if the money inside your card is enough for all the snacks. So, you decided to design a calculator to help you check if the card is valid and how many snacks you can buy.

#### ✓ Description of this lab

##### ➤ Input:

You will receive a number, `card_num`(64 bits), as the credit card number, representing 16 numbers(range from 0~9) of the credit card(4 bits/digit). The parameter "input\_money" (9 bits) represents how much money is inside the credit card. Also, a number, `snack_num` (32 bits), will represent 8 different types of snacks' amount needed(4 bits/each), and the variable price (32 bits) represents the price of each snack(4 bits/each).

- [63:0] `card_num` => 16 digit, 4 bits each.
- [8:0] `input_money`
- [31:0] `snack_num` => 8 different snacks, 4 bits each.
- [31:0] `price` => 8 different price, 4 bits each.

##### ➤ Calculate Card Number

First, you must check if the credit card number is valid. The credit card number checking rule is as follows.

- Step 1. => lookup table

Multiply all the odd digits by 2, separate all the digits after multiplying them, and sum it up.

(which means if the digit is 8 and 16 after multiplying, make it 1 and 6 separately)

➤ Step 2.

Add on the even digits.

➤ Step 3.

sum 0 sum 1 sum 2 sum 3 sum 4 sum 5 sum 6 sum 7

If the sum of all the digits can be divided by 10, then it's a valid number.

Even odd

card_num	[63:60]	[59:56]	[55:52]	[51:48]	[47:44]	[43:40]	[39:36]	[35:32]	[31:28]	[27:24]	[23:20]	[19:16]	[15:12]	[11:8]	[7:4]	[3:0]
Digit	4	0	4	8	0	2	2	2	0	7	8	6	8	1	3	4
multiply	8	x	8	x	0	x	4	x	0	x	16	x	16	x	6	x

$$\text{sum} = 8 + 0 + 8 + 8 + 0 + 2 + 4 + 2 + 0 + 7 + (1 + 6) + 6 + (1 + 6) + 1 + 6 + 4 = 70$$

$$70 \% 10 = 0 \Rightarrow \text{Valid number}$$

↓  
odd  
digit

➤ Buy Snack

After checking the credit card number, you can now start to buy the snacks.

Buy them from the highest total price until you can't buy them anymore. Be sure that you can only buy the required amount of snacks. If the money is not enough to buy the exact amount, then you don't need to buy it.

Ex: You have 450 dollars (input\_money = 450)

priority encoder

sub\_temp 0

	snack_num	price	total	Buy
1	[31:28]	15	15	Yes
2	[27:24]	3	6	No
3	[23:20]	7	8	No
4	[19:16]	13	10	Yes
5	[15:12]	6	1	No
6	[11:8]	12	7	Yes
7	[7:4]	10	4	No
8	[3:0]	4	4	No

$$\text{Total cost} = 225 + 130 + 84 = 365$$

➤ Calculate & Output

There are two output signals, "out\_valid" and "out\_change".

➤ out\_valid: If the credit card number is valid, out\_vlaid should be 1, else is 0.

- out\_change: If the credit card number is **invalid**, out\_change should be the **same as input\_money**. Otherwise, **output the change** after you have bought the snacks.

Example 1:

Credit card number(card\_num): 1234 1234 1234 1234

Input money(input\_money): 400

Snacks needed(snack\_num): 1, 2, 3, 4, 5, 6, 7, 8

Snacks' price(price): 8, 7, 6, 5, 4, 3, 2, 1

**out\_valid: 0 (credit card number invalid)**

out\_change: 400

Example 2:

Credit card number(card\_num[0]~[15]): 4556 4976 7312 5561

Input money(input\_money): 100

Snacks needed(snack\_num[0]~[7]): 1, 2, 3, 4, 5, 6, 7, 8

Snacks' price(price[0]~[7]): 8, 7, 6, 5, 4, 3, 2, 1

out\_valid: 1

out\_change: 10 (100 - 20 - 20 - 18 - 18 - 14 = 10)

The summary of the description and specifications are as followings:

Input Signal	Bit Width	Description
card_num	4 / each (with 16 digits) Total 63 bits	ranged from <b>1~9</b> (a digit) <b>unsigned integer</b>
input_money	9	ranged from <b>1~511</b> <b>unsigned integer</b>
snack_num	4 / each (with 8 different type) Total 32 bits	ranged from <b>1~15</b> (each type) <b>unsigned integer</b>
price	4 / each (with 8 different price) Total 32 bits	ranged from <b>1~15</b> (each price) <b>unsigned integer</b>


Output Signal	Bit Width	Description
out_valid	1	“1” when the credit card number is valid, else “0”.
out_change	9	The change after buying the snacks from the highest total price to the lowest one. Keep the same as “input_money” if the credit card number is <b>invalid</b> .

### Specifications

1. Top module name : SSC(File name: SSC.v)
2. After synthesis, check the “SSC.area” and “SSC.timing” in the folder “Report”. **The area report is valid only when the slack in the end of “SSC.timing” is “MET”.**
3. The synthesis result **cannot** contain any **latch**.

**Note:** You can check if there is a latch by searching the keyword “**Latch**” in 02\_SYN/syn.log

### Block Diagram

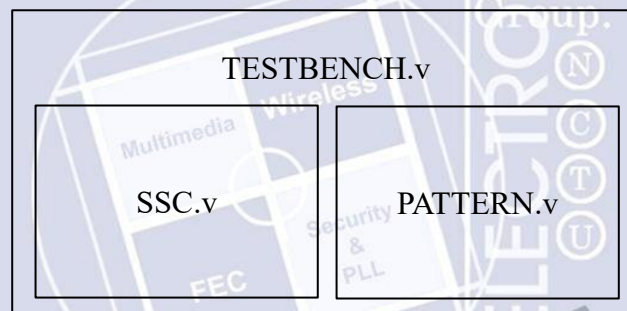

### Grading Policy

The performance is determined by the area of your design. The less area your design has, the higher grade you get. Try to reach better performance by thinking your architecture before coding.

Function Validity: 70%

Performance: area 30%

If you fail Lab01 at the first demo and pass at the second demo, you will get 30% off of your original score. Get no score if you fail both the first and second demos. Note that you will get **a 0 score if you are found plagiarism in your code**.

## Note

1. Tar all your design by run the command **Lab01/09\_SUBMIT/00\_tar**
2. Submit your design through **Lab01/09\_SUBMIT/01\_submit**
  - a. 1st\_demo deadline: **2023/09/18(Wed.) 12:00:00**
  - b. 2nd\_demo deadline: **2023/09/20(Fri.) 12:00:00**
3. If your file **violates the naming rule**, you will **lose 5 points**.
4. Don't use any wire/reg/submodule/parameter name called **\*error\***, **\*Congratulations\***, **\*latch\*** or **\*FAIL\*** otherwise you will fail the lab. Note: \* means any char in front of or behind the word. e.g: error\_note is forbidden.

Be careful about all details!

Template folders and reference commands:

In demo, the reference commands is:


1. 01\_RTL (RTL simulation):  
**./01\_run\_vcs\_rtl**
2. 02\_SYN/ (Synthesis):  
**./01\_run\_dc\_shell**  
(Check **latch** by searching the keyword "**Latch**" in 02\_SYN/syn.log)  
(Check the design's timing in /Report/ SSC.timing)  
(Check the design's area in /Report/ SSC.area)
3. 03\_GATE/ (Gate-level simulation):  
**./01\_run\_vcs\_gate**
4. **09\_SUBMIT/ (submit your files):**  
**./00\_tar**  
**./01\_submit**  
**./02\_check**

You can key in **./09\_clean\_up** to clear all log files and dump files in each folder
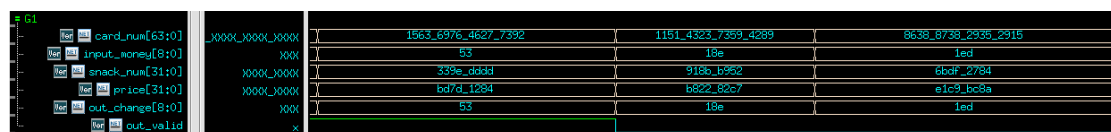
## Example Waveform

Input and output signal:

\* all the input and output are shown in hexadecimal \*



## Hint

---

**Hint1:** Try to use **behavior modeling description** instead of gate level description.

**Hint2:** Try to use **submodule** rather than copy and paste to simplify your design. (not necessary in this lab)

```
// -----  
// Example for using submodule  
// BBQ bbq0(.meat(meat_0), .vagetable(vagetable_0), .water(water_0),.cost(cost[0]));  
// -----
```

**Hint3:** Try to think if there is any possible **hardware** that can be **shared** with different mode operation. You can use command `dc_shell-gui` to examine your design.(not necessary in this lab)

**Hint4:** Pattern provided by TA will cover **only some simple cases**, you can try to write **your own input / output file** by yourself. Here is the format how TA will read in PATTERN:

```
/* input.txt format  
1. [PATTERN_NUM]  
  
repeat(PATTERN_NUM)  
    1. [card_num_0] [card_num_1] ... [card_num_15]  
    2. [input_money]  
    3. [snack_num_0] [snack_num_1] ... [snack_num_7]  
    4. [price_0] [price_1] ... [price_7]  
*/  
  
/* output.txt format  
1. [out_valid]  
2. [out_change]  
*/
```

You can check input.txt and PATTERN.v in 00\_TESTBED as a reference, and choose to write either c++/python or Verilog code for generating corner cases.